

$V_{GB} \rightarrow$  Unity Gain Bandwidth.

AT WH

$$A_D = -\frac{R_F}{R_1} V_{in} \Rightarrow B = 1/A_D$$

$$A_D = \left(1 + \frac{R_F}{R_1}\right) (V_{in}) \Rightarrow B = 1/A_D$$

$$R_{OF} = \frac{R_O}{1 + A_D} \Rightarrow R_{OF} = \frac{R_O}{1 + A/A_D}$$

$$f_1 = \frac{V_{GB}}{A_D}$$

Q.1) For a diff amp in 2 opamp confign  
 $R_1$  &  $R_3$  are  $= 680 \Omega$ ,  $R_F$  &  $R_2 = 6.8 \text{ k}\Omega$   
 $V_{in} = 1.5 \text{ V}$  at  $f_{in} = 1 \text{ kHz}$  then  
 741C find out the vltg gain, i/p  
 resistance, o/p resistance, o/p vltg for  
 the amp.

$$\begin{aligned} \rightarrow A_D &= -\frac{R_F}{R_1} V_{in} \\ &= \frac{6.8 \times 10^3}{680} = 10 \\ &= 1 + \frac{6.8 \times 10^3}{680} = 11 \end{aligned}$$





Saturation level =  $\pm 14$


O/p signal come in  $+14$  to  $-14$  b/w  $\curvearrowright$

No.


Date / /

\* Inverting amplr:-

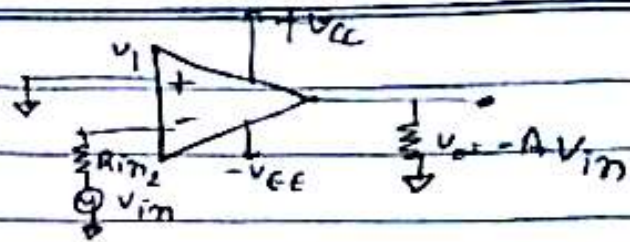- sign  $\rightarrow$  o/p is  $180^\circ$  phase shift or reciprocal



\* Non-inverting amplr:-

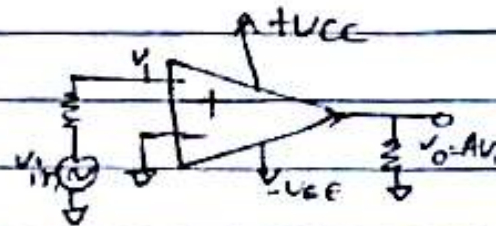

Q.1]

Determine the o/p vltg for open loop differential amplr if (a)  $V_{in1} = 5 \mu V$  dc  $V_{in2} = -7 \mu V$  dc

(b)  $V_{in1} = 10 \text{ mV rms}$   $V_{in2} = 20 \text{ mV rms}$

opamp is a  $741$  with a following specifications-

The gain of the opamp  $A = 2 \times 10^5$ ,  $R_{in} = 2 \text{ M}\Omega$ ,

$R_o = 75 \Omega$ ,  $+V_{cc} = +15 \text{ V}$ ,  $-V_{ee} = -15 \text{ V}$ .

$\rightarrow$  ~~Given~~  $A = 2 \times 10^5$ ,  $R_{in} = 2 \text{ M}\Omega$

$R_o = 75 \Omega$ ,  $+V_{cc} = +15 \text{ V}$ ,  $-V_{ee} = -15 \text{ V}$

$$A = \frac{V_o}{V_{id}} \Rightarrow V_{id} = V_1 - V_2$$

$$= R_{in} = 2 \text{ M}\Omega$$

$$R_{in} = R_1 - R_o$$

$$2 \times 10^6 = R_1 - 75$$

$$R_1 = 2 \times 10^6 + 75 = 2.00 \times 10^6$$

$$V_{id} = V_{in1} - V_{in2} = 10 - 20 = -10 \text{ mV}$$


$$A = \frac{V_o}{V_{id}} \Rightarrow 2 \times 10^5 = \frac{V_o}{-10} \Rightarrow V_o = -24$$



IFC

21/07/17  
Friday.

Q. ckt of opamp: -

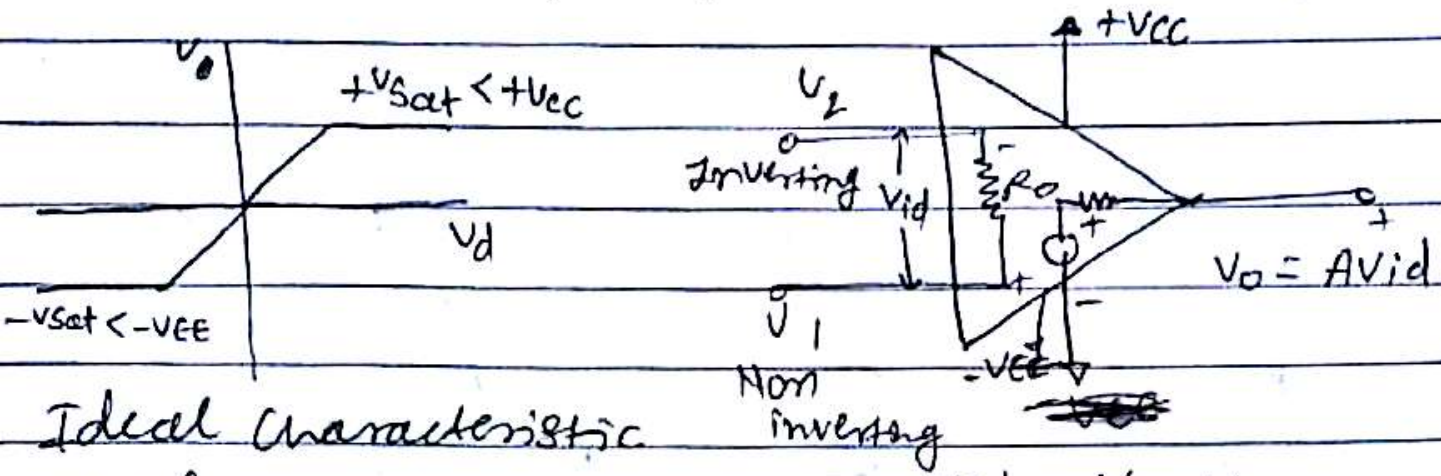

Ideal characteristic  
curve of op-amp

$$V_{id} = V_1 - V_2$$

$$V_0 - I_0 R_0 - A V_{id} = 0$$


$$V_0 = A V_{id}$$

diff b/w inverting & non-inverting  
the o/p also

$$V_0 = A V_{id} \Rightarrow \boxed{A = \frac{V_0}{V_{id}}} \rightarrow \text{gain of the amplifier.}$$

Q. Differential amplifier:-

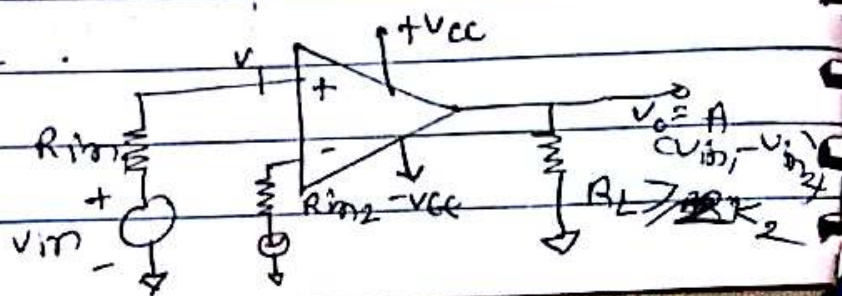For amplification of AC  
as well as DC we used  
diff. amplifier.





श्वेता

SHWETA


$$V_{sd} = V_1 - V_2 = 0 - V_f = -V_o = -\frac{V_o - A_{vd} V_o}{R_f} \quad \text{--- (1)}$$

$$V_{id} = V_1 - V_2 = 0 - V_f = -\frac{R_1}{R_1 + R_f} V_o = -B V_o$$

$$\text{--- } B V_o \text{ put in (1) } \Rightarrow -V_o = \frac{V_o + A_{vd} B V_o}{R_o}$$

$$R_{of} = \frac{V_o}{I_o} \Rightarrow R_{of} = \frac{V_o}{\frac{V_o}{R_o} (1 + A_{vd} B)}$$


### Bandwidth with Feedback :-

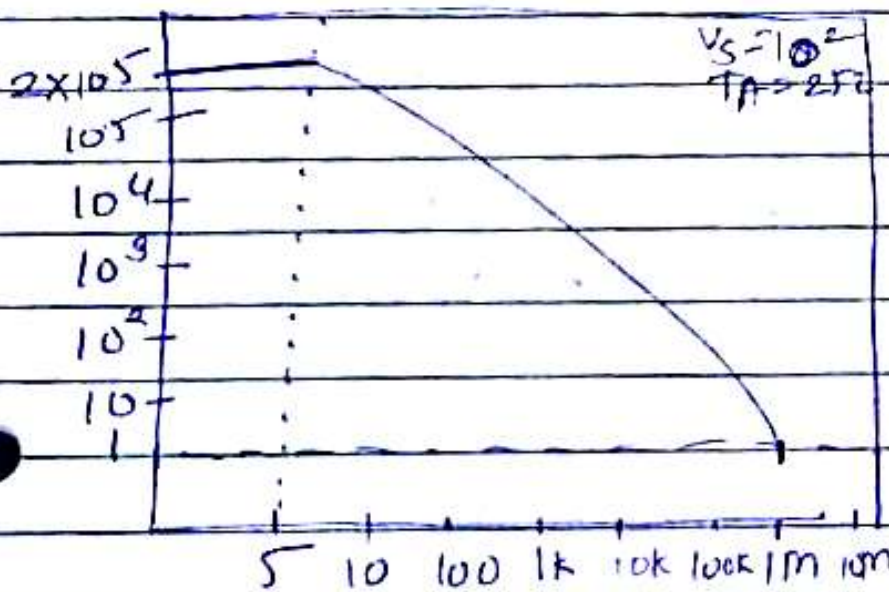


(freq) Hz.

The gain BW product is defined for opamp 741 which is product of BW & gain. So for 741 amp we have one bandwidth freq. below unity gain BW. The bandwidth defined as freq. where gain is 3dB down from the value at 0 Hz.
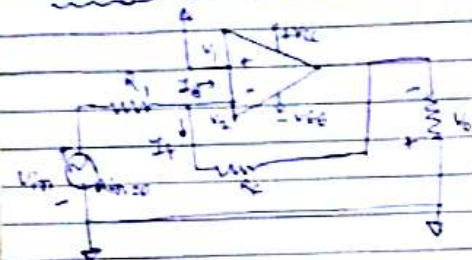
### \* Voltage Shunt Feedback Amplifier:-


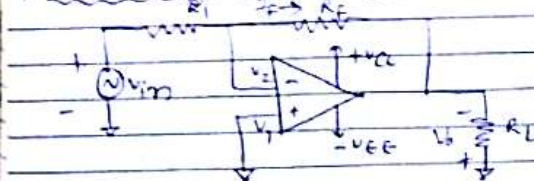
### \* Inverting Amplifier with \$-VE\$ f/b Vtg Shunt:-



Close loop gain of inverting amplifier

$$I_{in} = I_B + I_F$$

\$R\_1\$ is very large so ignore \$I\_B\$

$$I_{in} = I_F$$

$$\frac{V_{in} - V_2}{R_1} = \frac{V_2 - V_o}{R_F} \quad \text{--- (1)}$$

$$V_o = A(V_1 - V_2)$$

$$V_1 = 0 \quad V_o = A(0 - V_2) \Rightarrow V_2 = \frac{V_o}{A}$$

Putting the value of \$V\_2 = \frac{V\_o}{A}\$ in eq. (1)

$$A_F = \frac{V_o}{V_{in}} = \frac{-A R_F}{R_1 + R_F + A R_1} \quad \text{exact}$$

$$A R_1 \gg R_1 + R_F$$

$$A_F = \frac{-A R_F}{A R_1} \Rightarrow A_F = \frac{-R_F}{R_1} \quad \text{Ideal}$$

\$A\_F < 1 \rightarrow\$ possible in inverting amplifier

\$A\_F < 1 \rightarrow\$ Not possible in non inverting amp

$$A_F = A \frac{R_F}{R_1 + R_F}$$

$$\frac{R_1 + R_F}{R_1 + R_F} + \frac{A R_1}{R_1 + R_F}$$

$$B A_F = \frac{A K}{1 + A B} \quad \left\{ \begin{array}{l} K = \frac{R_F}{R_1 + R_F} \\ B = \frac{R_1}{R_1 + R_F} \end{array} \right.$$

Is the gain of the inverting amplifier

is the \$K\$ times of non inverting amplifier

where, \$K < 1\$.

gain of the inverting amplifier \$\rightarrow\$ gain of the non inverting amplifier.



For a 741 opamp having the foll. parameters connected to non inv. amp. with the value of  $R_f$  &  $R_i$  given.

$$R_i = 1k\Omega, R_f = 10k\Omega, A = 2 \times 10^5,$$

$$R_i = 2M\Omega, R_o = 75\Omega, f_o = 5Hz,$$

$$\text{Supply } V_{OH} = \pm 15V$$

$$\text{Find } A_f, R_{if}, R_{of}, f_i = V_{OOT}$$

$$A_f = \frac{A}{1+AB} = \frac{2 \times 10^5}{1+2 \times 10^5}$$

$$A_f = \frac{A(R_i + R_f)}{R_i + R_f + AR_i}$$

$$= \frac{(2 \times 10^5)(1 \times 10^3 + 10 \times 10^3)}{1 \times 10^3 + 10 \times 10^3 + (2 \times 10^5)(1 \times 10^3)}$$

$$= 10.99$$

$$\theta = \frac{R_i}{R_i + R_f} = 0.090$$

$$R_{if} = R_i(1+AB) = 1.0$$

$$R_{of} = \frac{R_o}{1+AB} = \frac{75}{1} = 75\Omega$$


$$f_i = f_o(1+AB) = 5Hz$$

$$V_{OOT} = \frac{V_o}{1+AB} = \frac{13}{(1+AB)} = 13V.$$



27/07/17  
Thursday

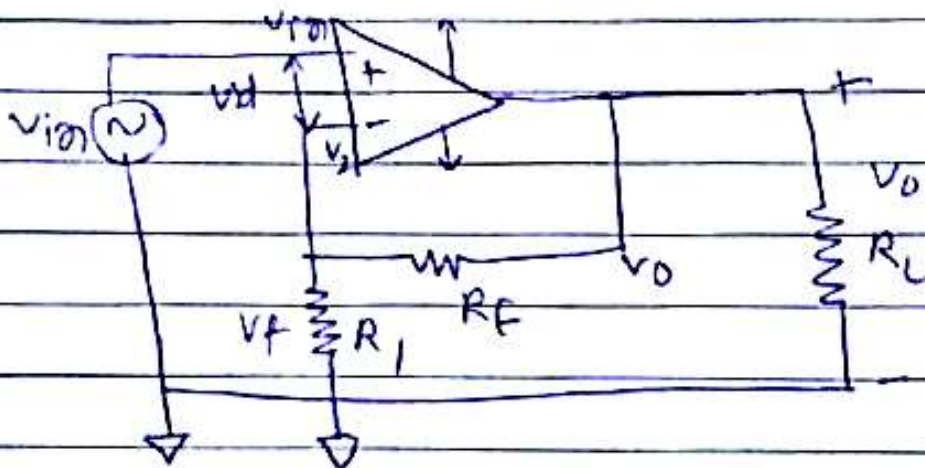\* opamp with negative feedback:-  
Non inverting configur<sup>n</sup> (Voltage series)



\* o/p loop is only suit to low freq.  
o/p vltg range ↑ o/p will clipped (limit)  
distortion in s/f.  
i.e. why o/p loop to close loop goes.

\* why we used -ve f/b

→ The f/b is subtracted from the i/p vltg.

$$V_o = A \times V_{id} = A(V_1 - V_2)$$

$$V_{in} - V_{id} - V_f = 0 \quad \dots \text{(by applying KVL)}$$

$$V_{id} = V_{in} - V_f$$

to reduce gain we used


-ve f/b purpose → to control gain & BW is increases.,



clp impedance & Non inverting > inverting

$$A_F = -\frac{K}{B}$$

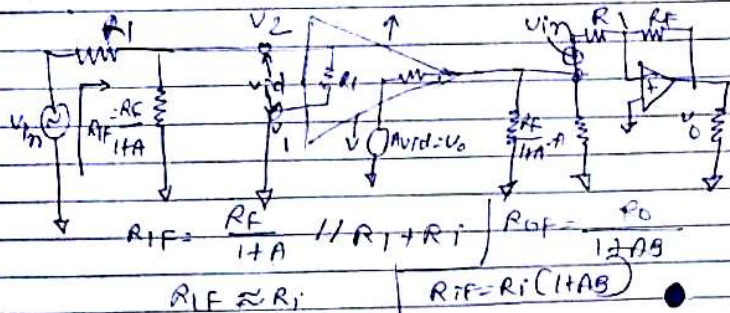Diff. clp is ideally zero  
 $V_{id} \approx 0 \Rightarrow V_1 - V_2 = 0$



$$R_{IF} \approx R_i$$

$$R_{IF} = R_i(1 + A_B)$$

the clp impedance of non inverting  
 flb amp > inverting flb amp  
 offset is same exactly as the  
 non inverting amp.



\* Bandwidth with feedback:-

$$f_F = f_0(1 + A_B)$$


$$V_{FB} = -I_{OA}$$

$$R_F = \frac{V_{FB} K}{A_F}$$

for non inverting  
 $R_F = \frac{V_{FB}}{A_F}$

clp offset vltg is same.

Differential amp with 2 opamps:-

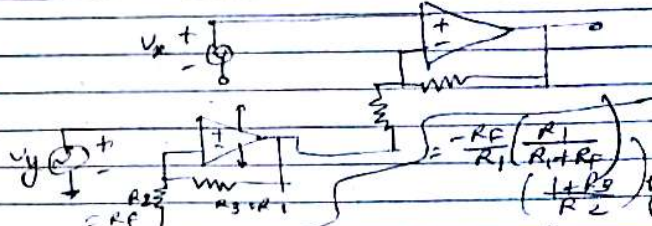

$$V_{01} = (1 + \frac{R_F}{R_1}) V_x$$

$$V_{02} = (1 + \frac{R_F}{R_2}) V_y$$

$$V_0 = V_{01} - V_{02}$$

$$V_0 = (1 + \frac{R_F}{R_1}) V_x - (1 + \frac{R_F}{R_2}) V_y$$

$$V_0 = \frac{R_F}{R_1} V_x - \frac{R_F}{R_2} V_y$$

$$= -\frac{R_F}{R_1} (H \frac{R_2}{R_2}) V_y$$

$$V_{01} + V_{02} = (1 + \frac{R_F}{R_1}) V_x$$

$$= \frac{R_F}{R_1} (1 + \frac{R_2}{R_2}) V_x$$

$$= (\frac{R_F}{R_1}) (V_x - V_y)$$

$$V_{GB} = A f_o \quad \text{--- (1)} \quad V_{GB} = A f + f \quad \text{--- (2)}$$

$$A f_o = A f \cdot f_f \Rightarrow f_f = \frac{A f_o}{A f} \quad A f = \frac{A}{1 + A B}$$

$$f_f = \frac{A f_o}{1 + A B} \Rightarrow \boxed{f_f = (1 + A B) f_o}$$

\* Voltage series non inverting conf. (-ve f/b)


$$1) A_f = \frac{A (R_1 + R_f)}{R_1 + R_f + A R_1} \quad \text{exact } A_f = \frac{A}{1 + A B}, \quad B = \frac{1}{A_f}$$

$$\text{ideal} = \left( 1 + \frac{R_f}{R_1} \right) \quad B = \frac{R_1}{R_1 + R_f} = \frac{V_f}{V_o}$$

$$2) R_{if} = R_i (1 + A B) \quad 4) f_{if} = f_o (1 + A B)$$

$$3) R_{of} = \frac{R_o}{1 + A B} \quad 5) V_{ootf} = \pm \frac{V_{od1}}{1 + A B}$$

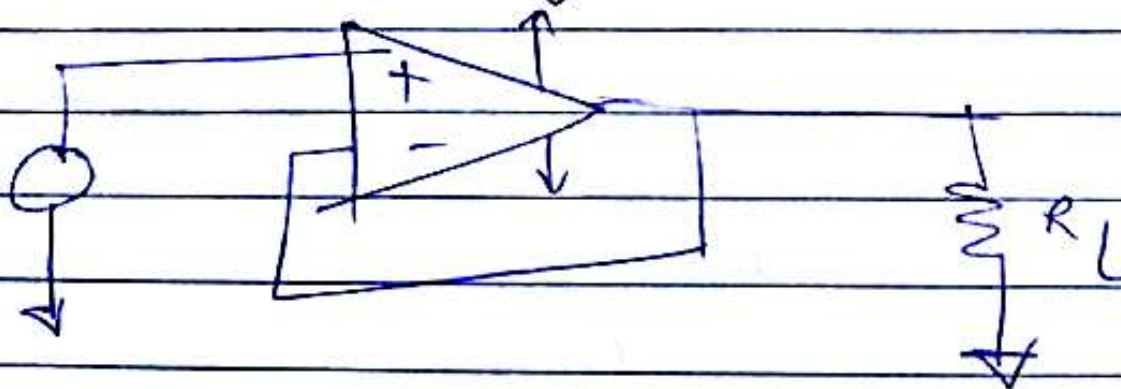Q.1) How the v/f follower can be designed from v/f series, non inverting conf. with -ve f/b.








IC

श्वेता SHWETA

20/07/19  
thursday

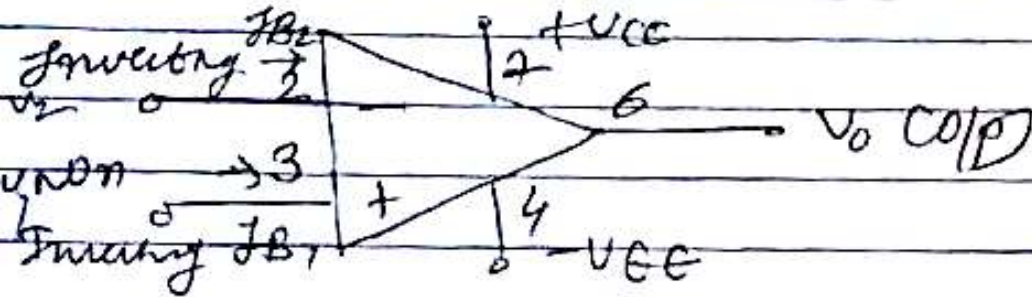\* Electrical characteristics of op-amp:-



$$V_{id} = V_1 - V_2$$

$$V = A \times V_{id}$$

$$V_o = A V_{id}$$

\* Input bias current =  $\frac{I_{B1} + I_{B2}}{2}$

CMRR =  $\frac{A_d}{A_{cm}}$  →  $\frac{\text{differential gain}}{\text{common mode gain}}$

$A_d$  → large signal gain

$A_{cm}$  → voltage very small

\* CMRR → good matching

\* CMRR should be very high.

A → o/p loop conf.  
A<sub>F</sub> → close loop conf.

B → gain.

2 → used  
No → 5V  
31 → 10V  
29 → 5V  
28 → 5V

**KPMG**  
 $\frac{V_f}{V_o} \rightarrow$  f/b gain of the ckt

$$V_o = A v_{id} = A(V_1 - V_2) = A(V_{in} - \frac{R_1}{R_1 + R_F} V_o)$$

$$\frac{V_o}{V_{in}} = A_F = \frac{A(R_1 + R_F)}{R_1 + R_F + AR_1}$$

... (If  $AR_1 \gg R_1 + R_F$ )

$\approx 1 + \frac{R_F}{R_1}$

$$A_F = 1 + \frac{R_F}{R_1}$$

Overall gain of non inverting opamp with -ve f/b.

$$A_F = \frac{A(R_1 + R_F)}{R_1 + R_F + AR_1}$$

Just divide num & deno by  $R_1 + R_F$

$$A_F = \frac{A(R_1 + R_F)}{(R_1 + R_F)}$$

$$\frac{R_1 + R_F}{R_1 + R_F} + \frac{AR_1}{R_1 + R_F}$$

$$A_F = \frac{A}{1 + AB}$$

\* Difference in put voltage ideally zero

$$V_1 = V_{in}$$

$$V_{id} = V_1 - V_2 = 0$$

$$V_2 = V_f = \frac{R_1}{R_1 + R_1} V_o$$

$$V_o = V_{in}$$